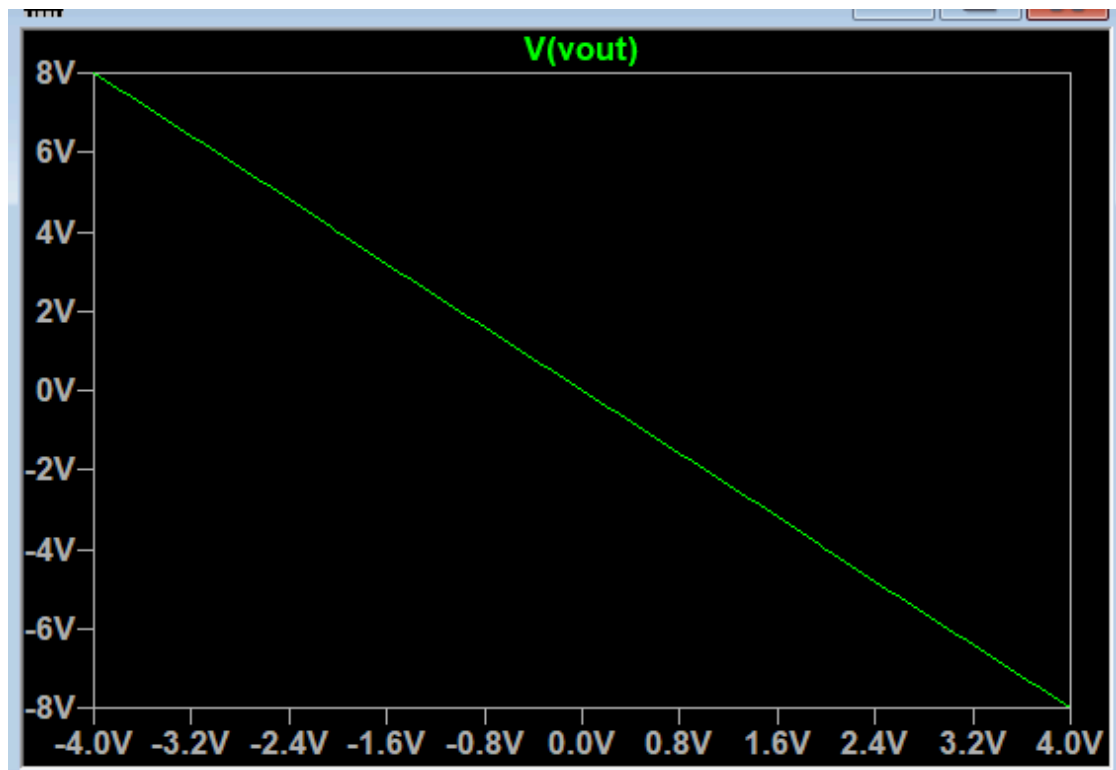



Part 1: VCVS



v_{out} vs v_{in} : The slope -2 is the VCVS's gain.

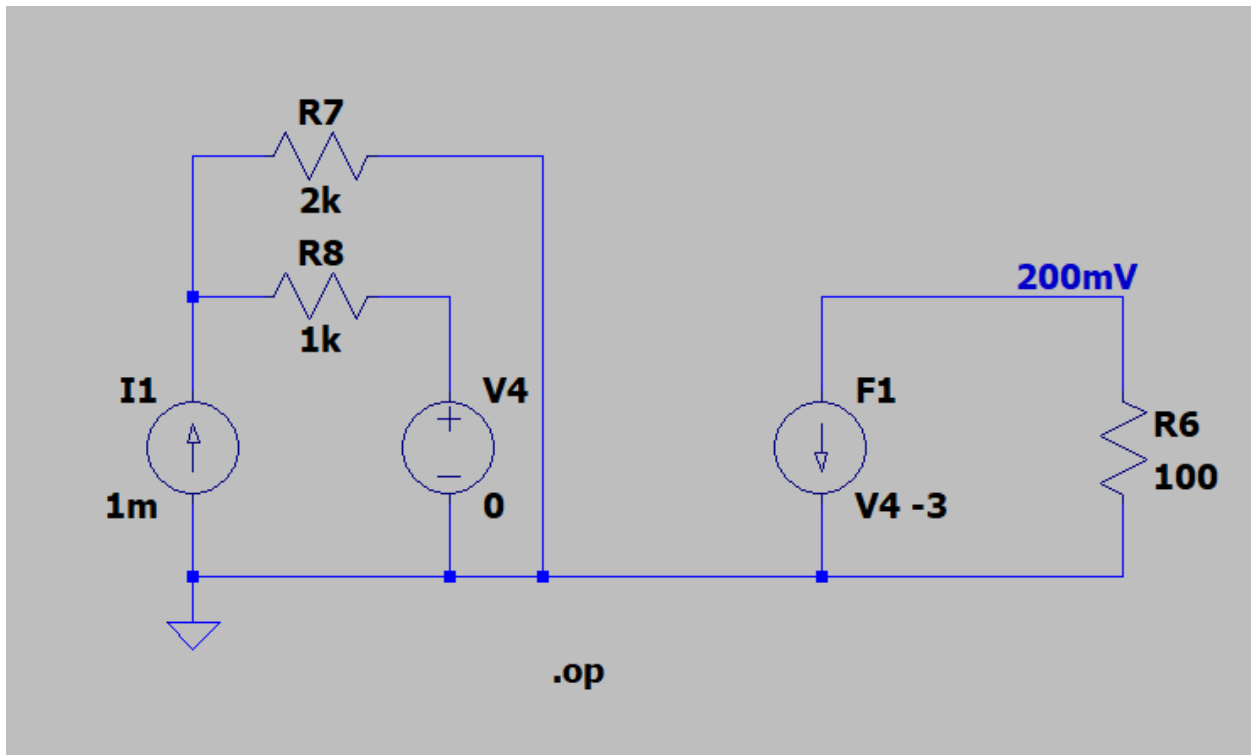Part 2: Current Controlled Devices

Modified CCCS circuit schematic that is -3x of the current in R8:



The updated .op label reading is 200 mV.

Double-check via the .op output:

```
* C:\Users\13764\Documents\LTspice\1.2.1.asc

--- Operating Point ---

V(n001) :      0.666667      voltage
V(n002) :      0           voltage
V(n003) :      0.2         voltage
I(F1) :      -0.002        device_current
I(I1) :      0.001         device_current
I(R8) :      -0.000666667  device_current
I(R7) :      -0.000333333  device_current
I(R6) :      0.002         device_current
I(V4) :      0.000666667  device_current
```

I (F1): -0.002

Part 3: VCVS Opamp Models


Let E be the VCVS gain.

Theoretical calculation:


$V_{out} = -E V_N$		$V_{in} = 1V:$	
$\frac{V_N - V_{in}}{1k} + \frac{V_N - V_{out}}{2k} = 0$		E	$V_{out} (V)$
$-\frac{2}{E} V_{out} - 2V_{in} - \frac{1}{E} V_{out} - V_{out} = 0$		75	-1.92308
$-2V_{in} = (1 + \frac{3}{E}) V_{out}$		1000	-1.99402
$V_{out} = -\frac{2E}{E+3} V_{in}$		1e5	-1.99994

VCVS .op simulation result:


E = 75, vout_nonideal = -1.9230769 V.

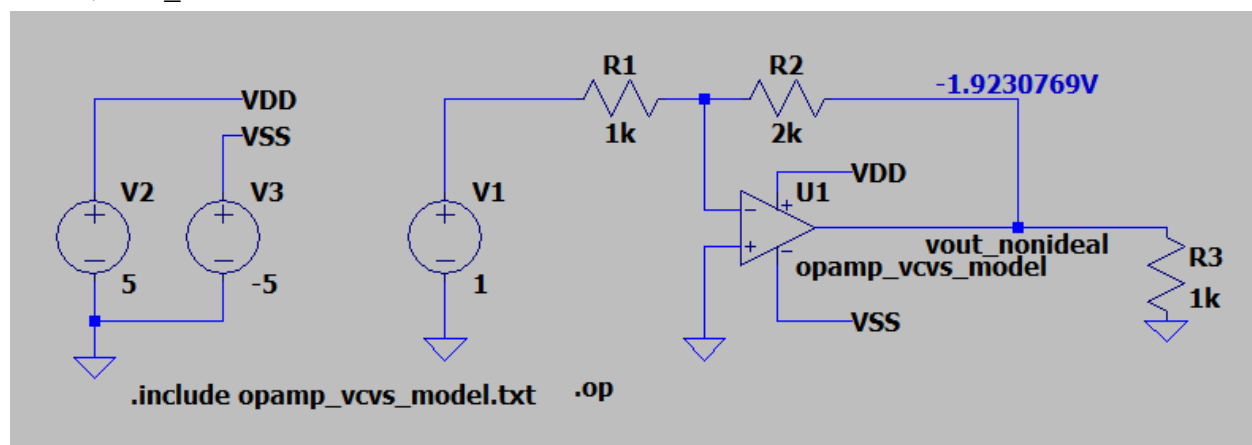

E = 1000, vout_nonideal = -1.9940179 V.

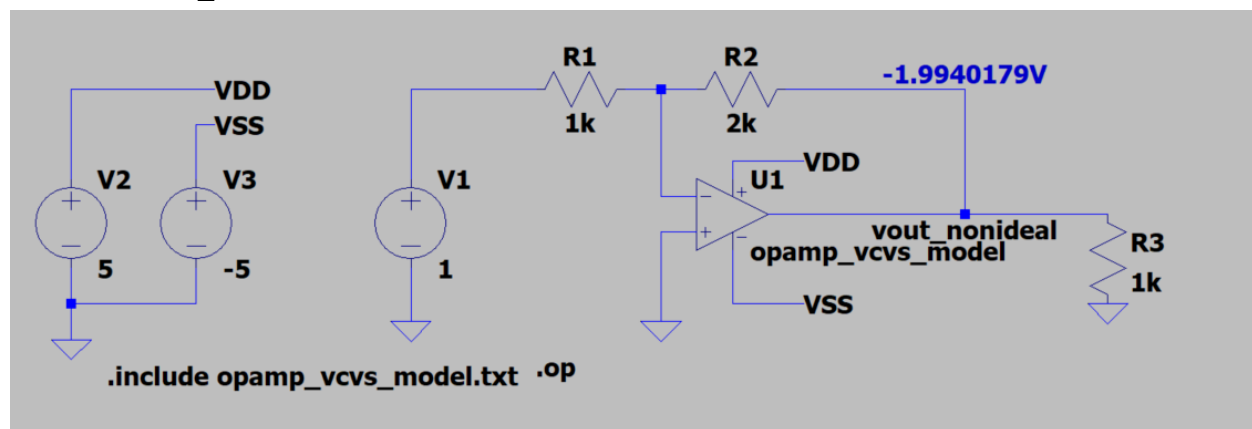

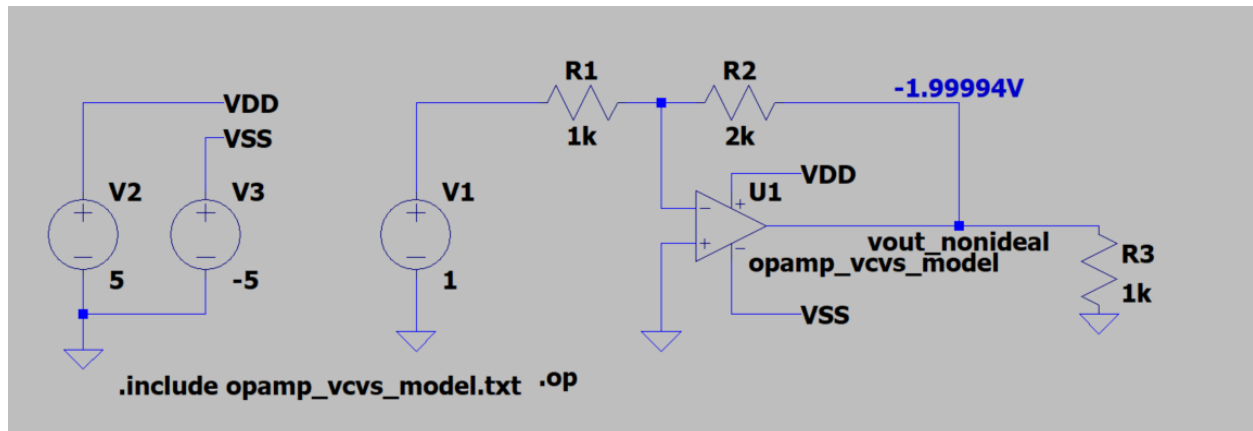$E = 1e5$, $v_{out_nonideal} = -1.99994 \text{ V}$



The calculation matches the simulation result exactly.

For an ideal opamp, where the open-loop gain is infinity, the gain is -2. The output should be -2 V when the input is 1 V. As the actual gain increases and approaches infinity, $v_{out_nonideal}$ approaches -2 V, closer to the ideal behavior

Part 4: Opamp with Saturation




v_{out} saturates at 5 V and -5 V due to the arctangent function.


Part 5: Commercial Opamp Model

LM741

DC sweep curve:

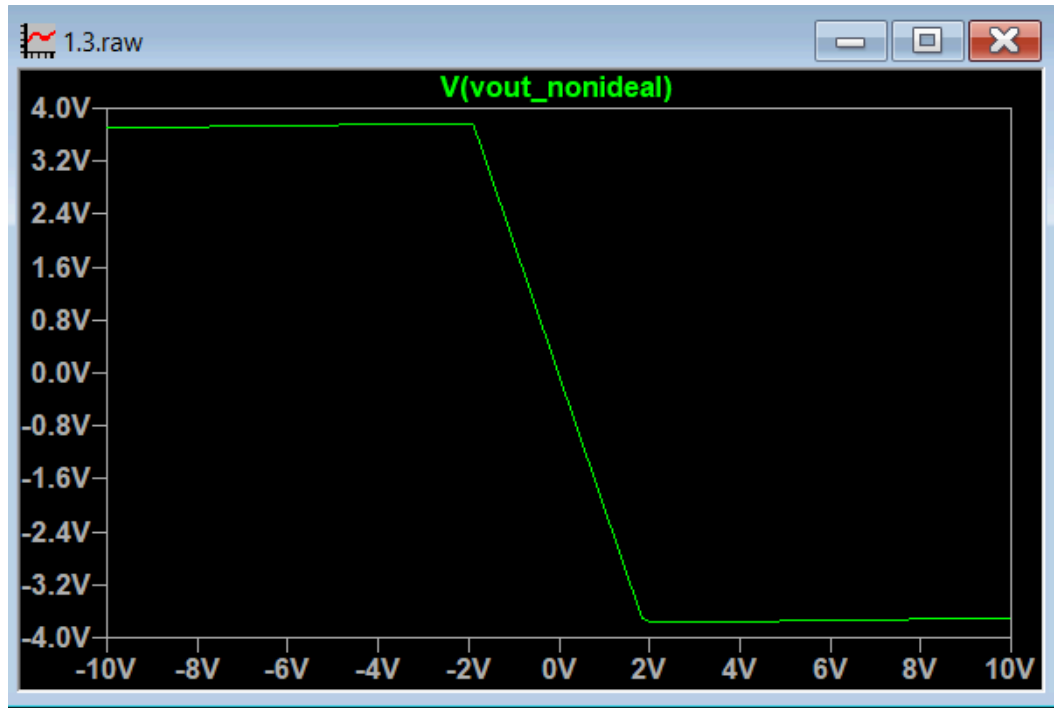

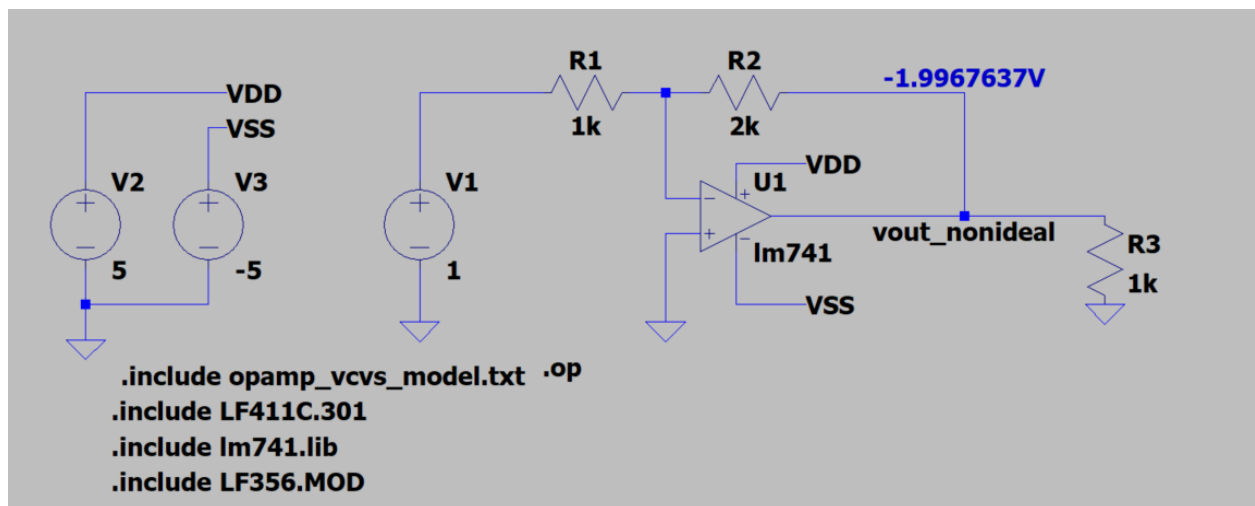
From the DC sweep curve, the output range is approximately -3.7 V to 3.7 V. The curve has sharp corners, very ideal.




vout_nonideal = -1.9967637 V, 99.84% of the ideal gain.

LF411C

DC sweep curve:

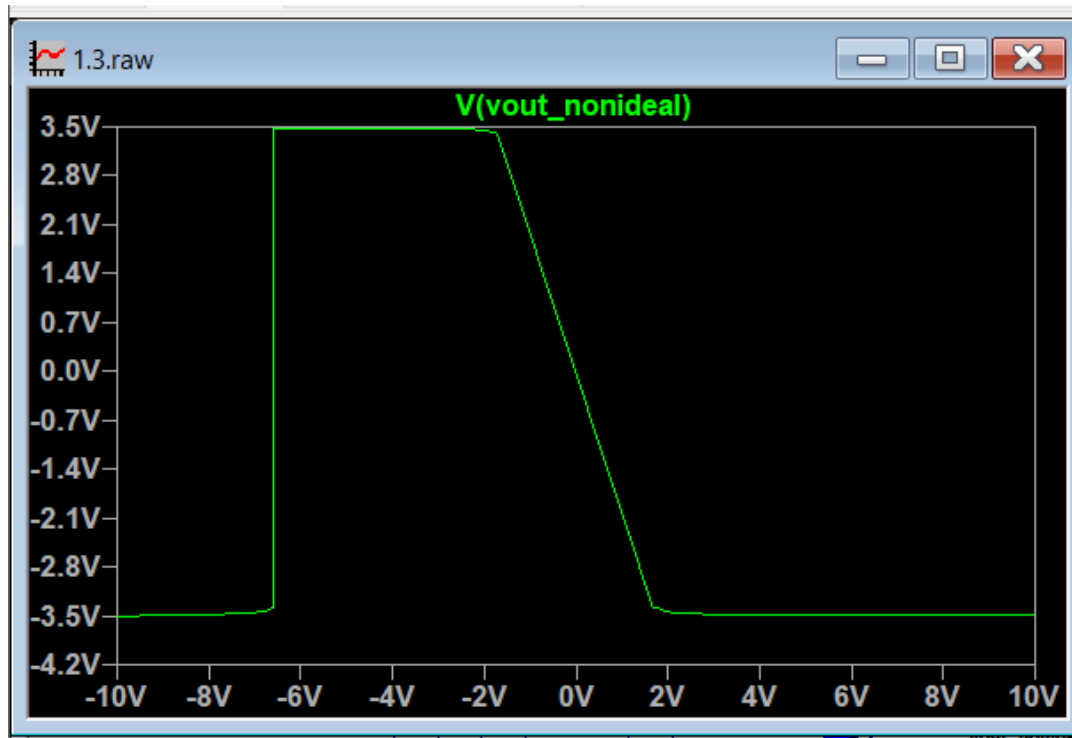

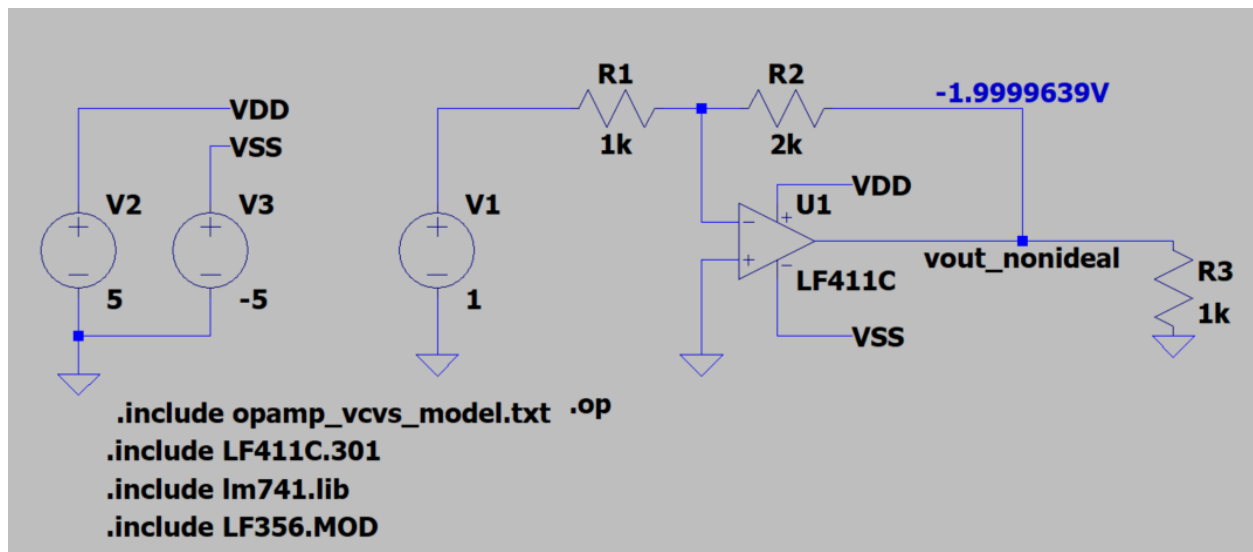
The output range is approximately -3.5 V to 3.5V. The corners are round, so there is some distortion before saturation. 1 V is in the linear region, so this does not affect our gain.




vout_nonideal = -1.9999639 V, 99.997% of the ideal gain

LF356/NS

DC sweep curve:

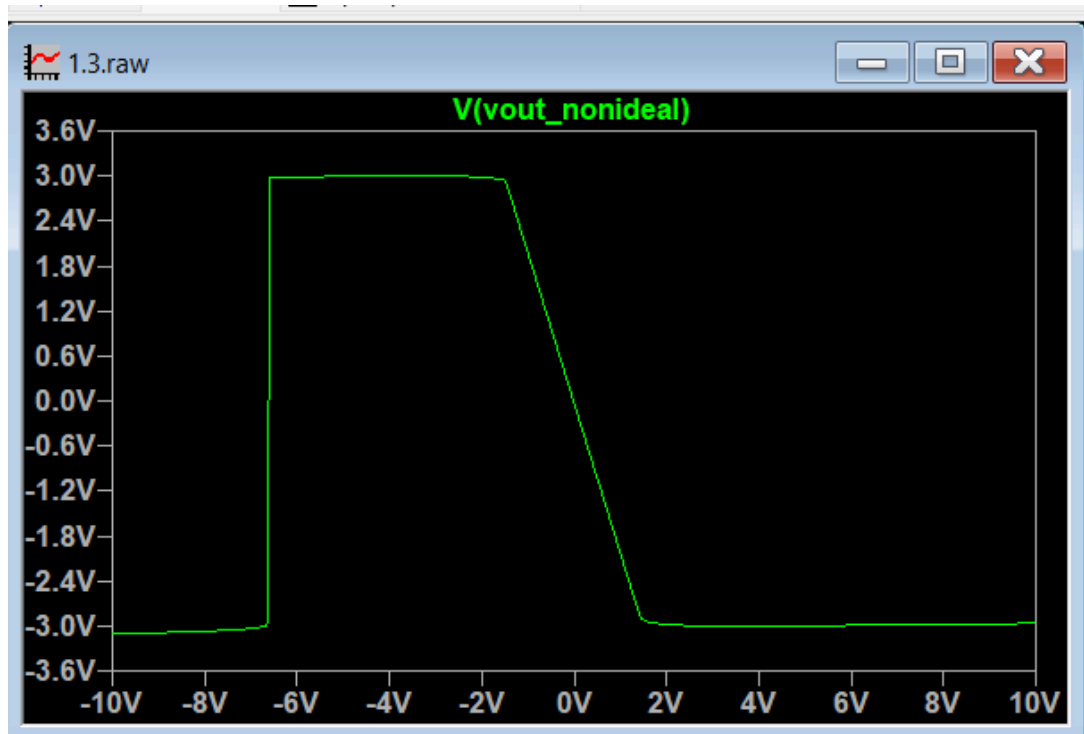

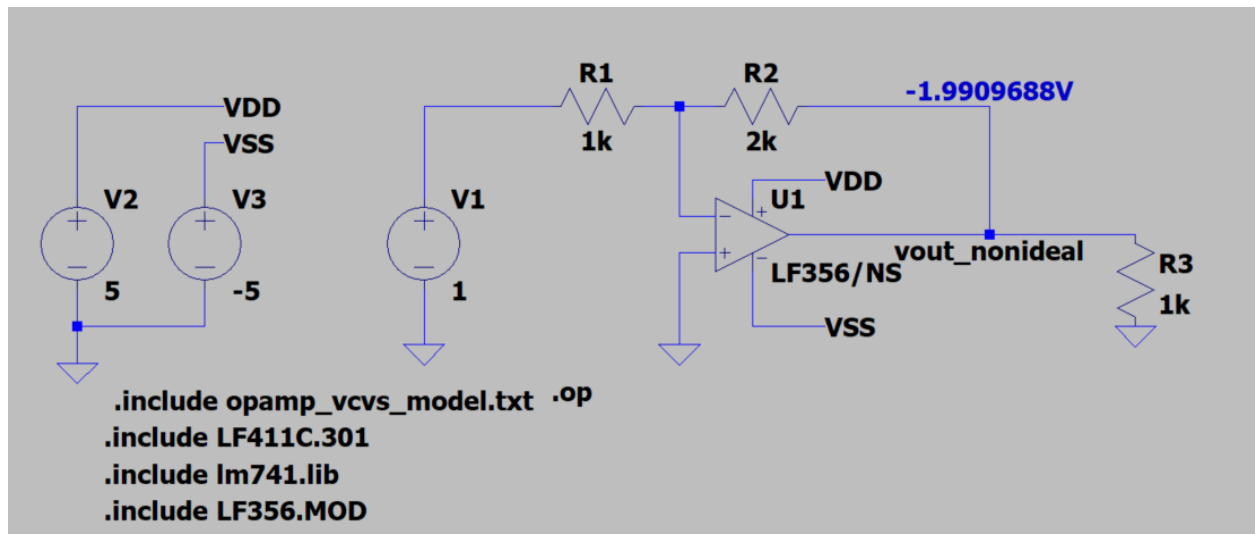
The output range is approximately -3 V to 3 V. Similar to LF411C, the corners are not sharp before saturation.



$v_{out_nonideal} = -1.9909688 \text{ V}$, 99.55% of the ideal gain.

Summary

Superimposing all three curves:

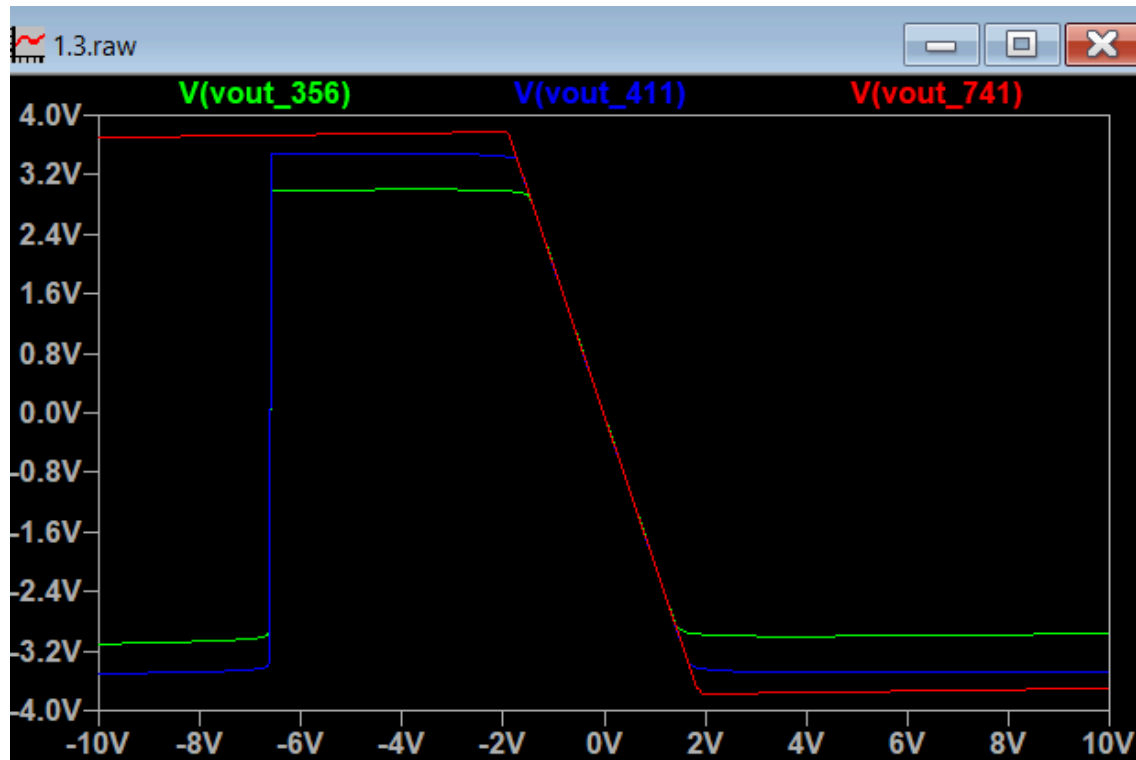


In terms of output voltage $vout_nonideal$ in the circuits above, LF411C's output is the closest to ideal, at 99.997% of the ideal gain.

In terms of DC sweep curve shape, LM741 gives the most ideal output. Its curve has sharper corners, so it still maintains an ideal (linear) output voltages close to saturation.

LM741 also gives the widest output range of approximately -3.7 V to 3.7 V.


Part 6: AC Analysis

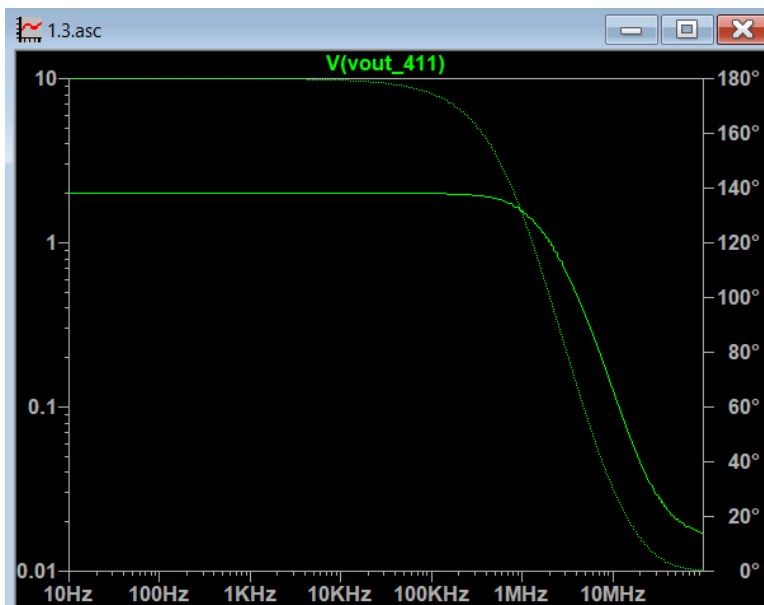

Above are the AC analyses of the four op amp models.

Summary

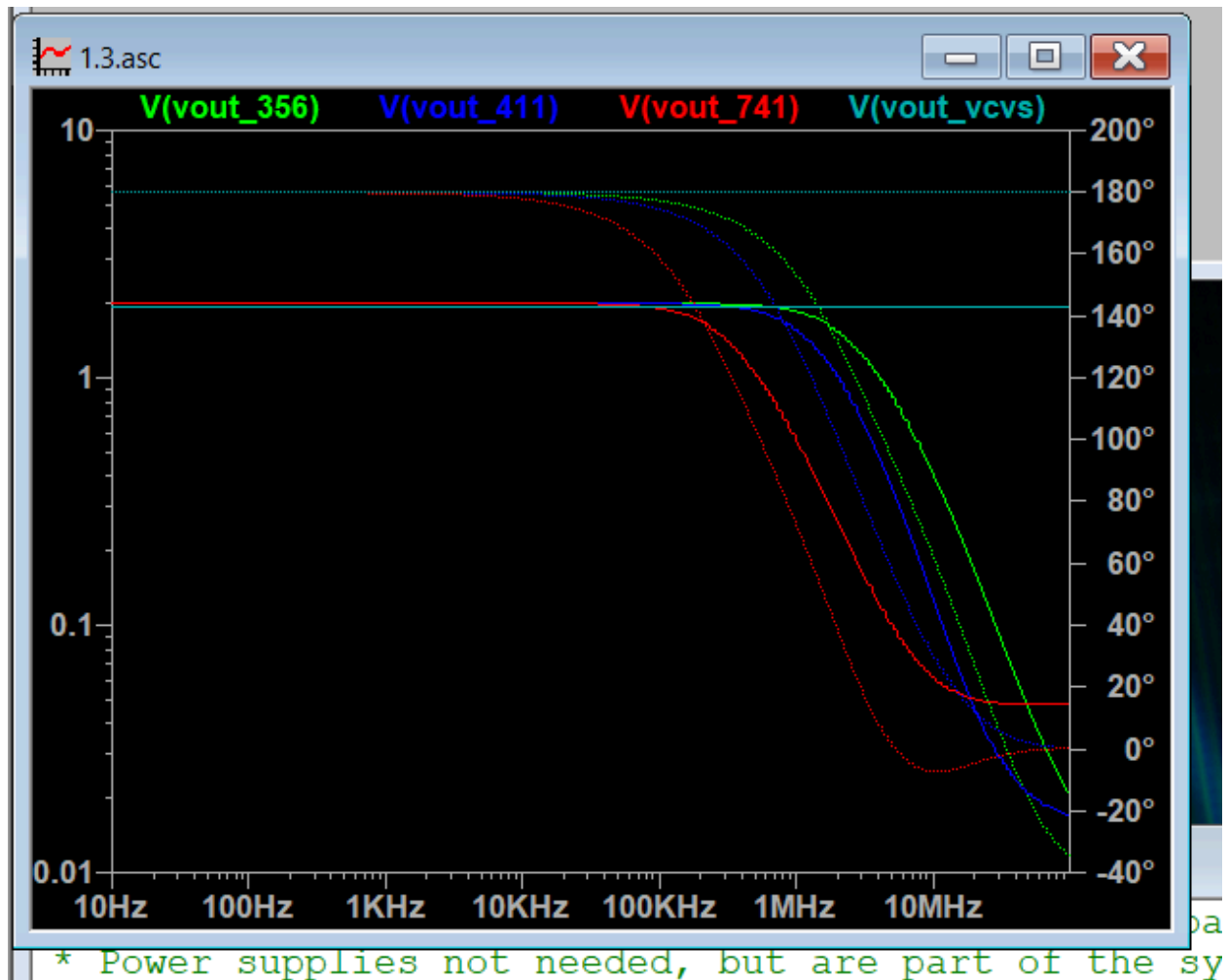
For comparison, I superimposed the four curves.




Among the commercial models, LF356 (green) has the widest frequency response, up to about 1 MHz, until the gain declines significantly below 2.

Part 7: Subcircuit


Subcircuit schematic:

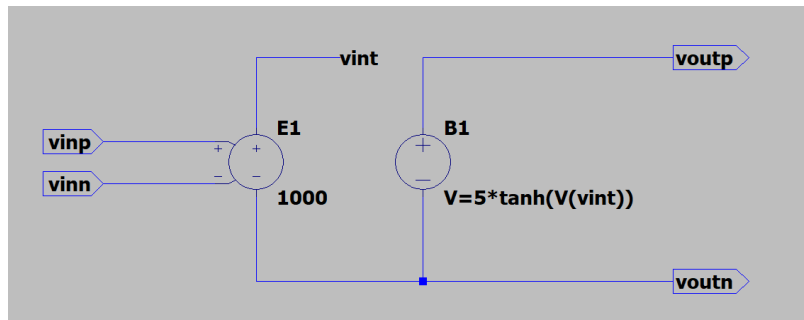

Subcircuit symbol:

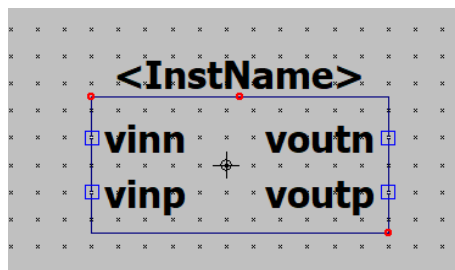

Circuit schematic:

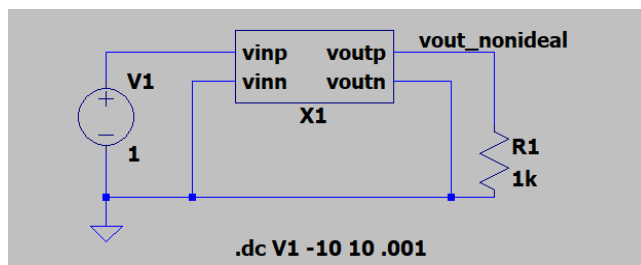

DC sweep plot:

